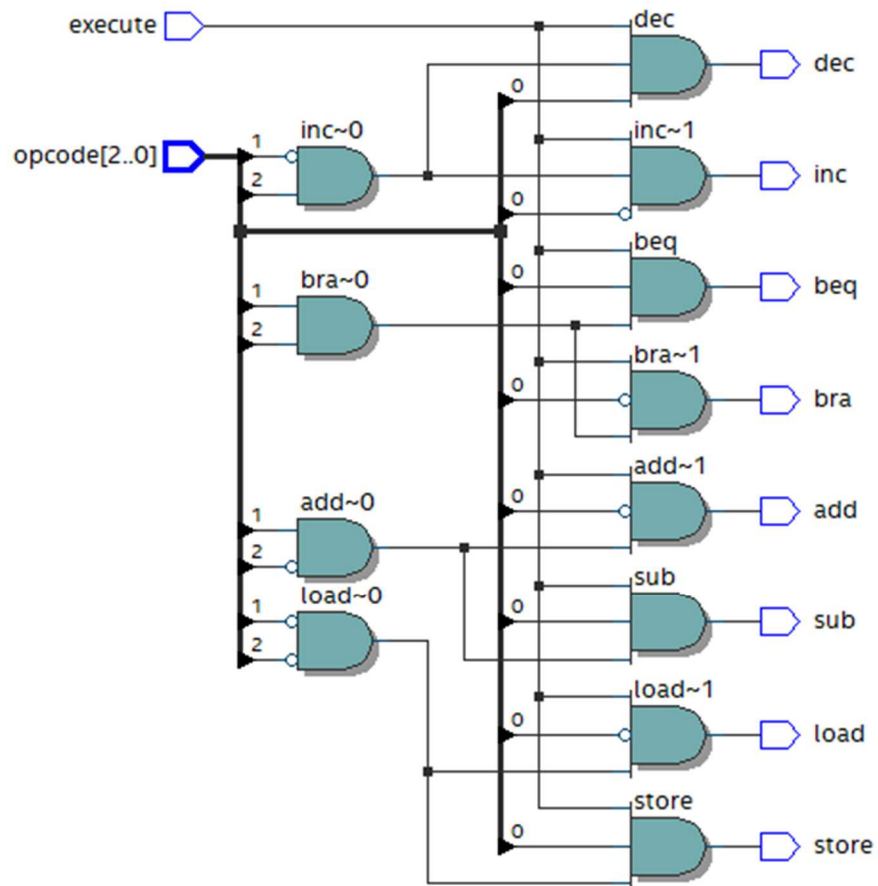


*Opcode Decoder Verification Report***Component****Figure 1: Opcode-Decoder Visual Schematic**

Opcode	Output
000	Load
001	Store
010	Add
011	Sub
100	Inc
101	Dec
110	Bra
111	Beq

**Figure 2: Mapping of Opcode to Output**

The purpose of this learning activity is to create a opcode-decoder combinational circuit where it takes in an input called *execute* and a bus with 3 digits called *opcode*. Whenever *execute* is 0, all outputs will print out 0. If *execute* is 1 then the affiliated *opcode* value will choose which output to send a signal of 1. Figure 1 illustrates the visual schematic of the opcode-decoder. Figure 2 shows the mapping between the opcode and the respective output.

### **Opcode-Decoder Signature**

#### **- INPUTS**

- Execute
- Opcode from 0 - 2

#### **- OUTPUTS**

- Load
- Store

- Add
- Sub
- Inc
- Dec
- Bra
- beq

## Verification Tests

Port Mapping  
 execute = execute\_tb  
 opcode[2..0] = opcode\_tb  
 load = load\_tb  
 store = store\_tb  
 add = add\_tb  
 sub = sub\_tb  
 inc = inc\_tb  
 dec = dec\_tb  
 bra = bra\_tb  
 beq = beq\_tb

execute_tb	opcode_tb	load	store	add	sub	inc	dec	bra	beq
0	000	0	0	0	0	0	0	0	0
0	001	0	0	0	0	0	0	0	0
0	010	0	0	0	0	0	0	0	0
0	011	0	0	0	0	0	0	0	0
0	100	0	0	0	0	0	0	0	0
0	101	0	0	0	0	0	0	0	0
0	110	0	0	0	0	0	0	0	0

0	111	0	0	0	0	0	0	0	0
1	000	1	0	0	0	0	0	0	0
1	001	0	1	0	0	0	0	0	0
1	010	0	0	1	0	0	0	0	0
1	011	0	0	0	1	0	0	0	0
1	100	0	0	0	0	1	0	0	0
1	101	0	0	0	0	0	1	0	0
1	110	0	0	0	0	0	0	1	0
1	111	0	0	0	0	0	0	0	1

**Figure 3: Truth Table of the Opcode-Decoder**




 


Figure 4: Verification Tests when *execute* = 0

 



 


Figure 5: Verification Test when *execute* = 1



```

# ** Note: Output correct for execute = 1 and opcode_tb = 000
#   Time: 10 ns   Iteration: 0   Instance: /testbench
# ** Note: Output correct for execute = 1 and opcode_tb = 001
#   Time: 20 ns   Iteration: 0   Instance: /testbench
# ** Note: Output correct for execute = 1 and opcode_tb = 010
#   Time: 30 ns   Iteration: 0   Instance: /testbench
# ** Note: Output correct for execute = 1 and opcode_tb = 011
#   Time: 40 ns   Iteration: 0   Instance: /testbench
# ** Note: Output correct for execute = 1 and opcode_tb = 100
#   Time: 50 ns   Iteration: 0   Instance: /testbench
# ** Note: Output correct for execute = 1 and opcode_tb = 101
#   Time: 60 ns   Iteration: 0   Instance: /testbench
# ** Note: Output correct for execute = 1 and opcode_tb = 110
#   Time: 70 ns   Iteration: 0   Instance: /testbench
# ** Note: Output correct for execute = 1 and opcode_tb = 111
#   Time: 80 ns   Iteration: 0   Instance: /testbench
# ** Note: Output correct for execute = 1 and opcode_tb = 000
#   Time: 90 ns   Iteration: 0   Instance: /testbench
# ** Note: Output correct for execute = 1 and opcode_tb = 001
#   Time: 100 ns  Iteration: 0   Instance: /testbench
# ** Note: Output correct for execute = 1 and opcode_tb = 010
#   Time: 110 ns  Iteration: 0   Instance: /testbench
# ** Note: Output correct for execute = 1 and opcode_tb = 011
#   Time: 120 ns  Iteration: 0   Instance: /testbench
# ** Note: Output correct for execute = 1 and opcode_tb = 100
#   Time: 130 ns  Iteration: 0   Instance: /testbench
# ** Note: Output correct for execute = 1 and opcode_tb = 101
#   Time: 140 ns  Iteration: 0   Instance: /testbench
# ** Note: Output correct for execute = 1 and opcode_tb = 110
#   Time: 150 ns  Iteration: 0   Instance: /testbench
# ** Note: Output correct for execute = 1 and opcode_tb = 111
#   Time: 160 ns  Iteration: 0   Instance: /testbench

```

**Figure 6: Verification Test Using Assert Statements**

Figures 4 – 6 display the verification and testing process of the opcode-decoder schematic. The test results in indicate that the schematic successfully passed according to the truth table in Figure 3. Therefore, the opcode-decoder schematic is correct and passed all the tests.