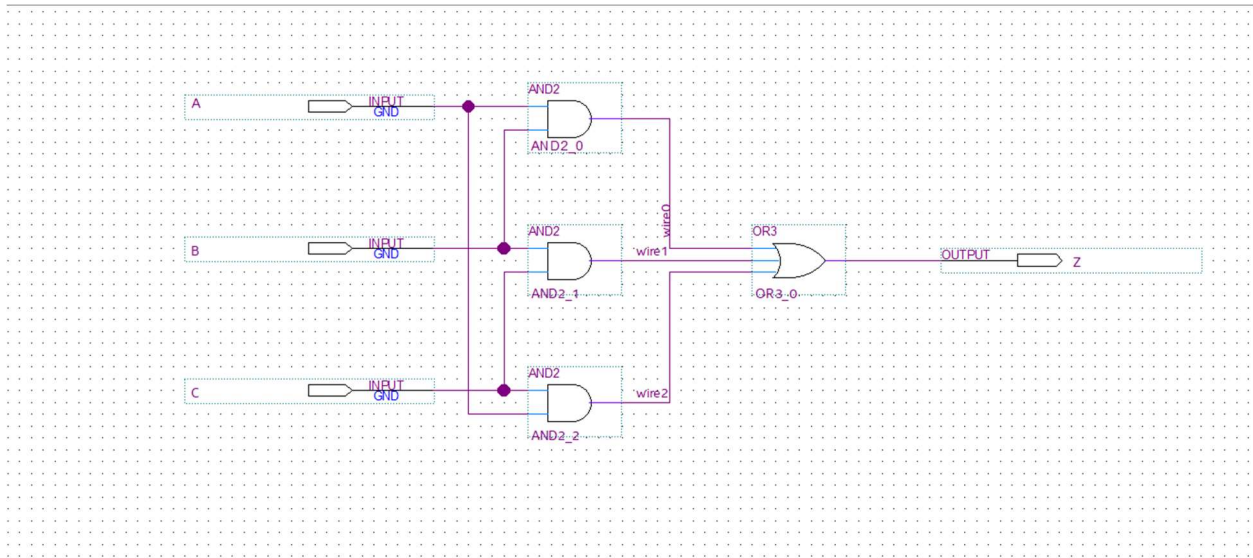


## Majority Voter Simulation Results

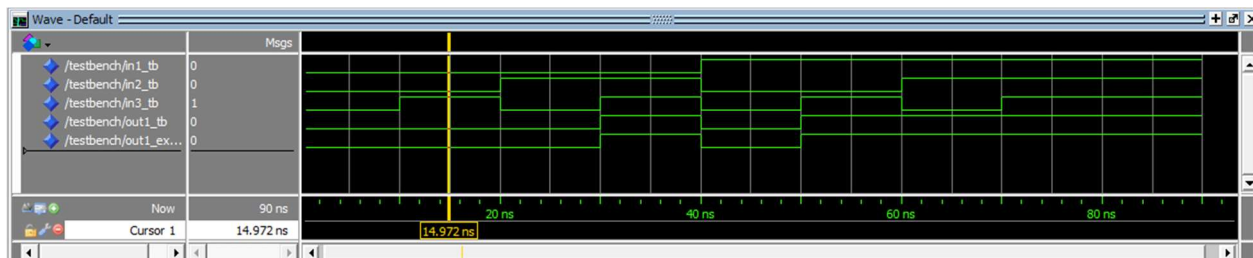
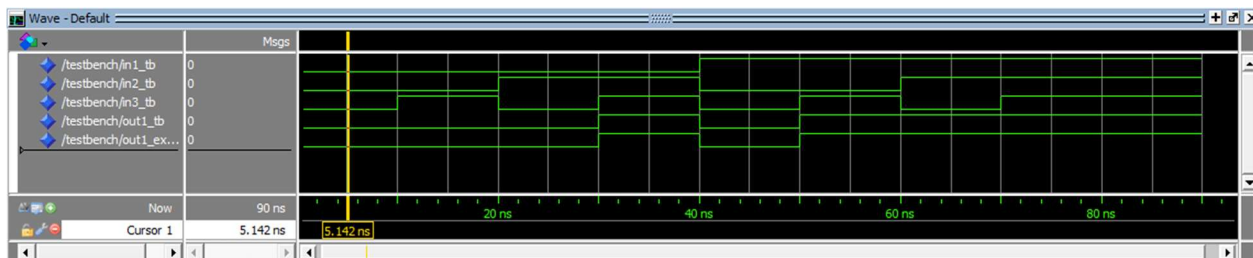
### Schematic



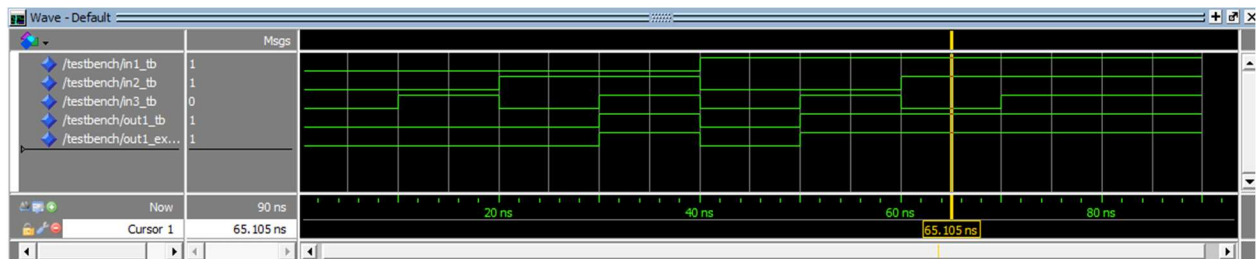
 


**Figure 1: Majority Voter Schematic**

The figure above illustrates the majority voter schematic which takes in the three inputs (A, B, C) and outputs the majority value (Z). In other words, two of the three inputs were 0 and the third was 1, then the output would be a 0 and vice versa.

### Verification Tests and Results

 

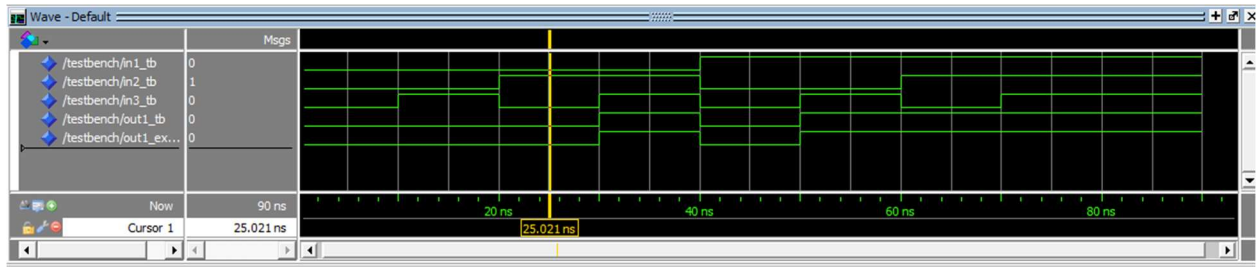



**Figure 2: Simulation Results for Verification**

The figure above illustrates the simulation results for the verification process. As indicated in the figure above, the actual output matches the expected output for all cases. A truth table of the majority voter schematic and the port mapping is provided below.

in1_tb	in2_tb	in3_tb	out1_tb	out1_expected
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

A = in1\_tb  
B = in2\_tb  
C = in3\_tb  
Z = out1\_tb

**Figure 3: Truth Table and Port Mapping**

The figure below illustrates the verification with assert statements.

```
# vsim work.testbench
# Start time: 14:27:44 on Sep 11,2022
# Loading std.standard
# Loading std.textio(body)
# Loading ieee.std_logic_1164(body)
# Loading work.testbench(gate_level)
# Loading work.majority_voter0(bdf_type)
# ** Note: Output correct for input = 000
#   Time: 10 ns Iteration: 0 Instance: /testbench
# ** Note: Output correct for input = 001
#   Time: 20 ns Iteration: 0 Instance: /testbench
# ** Note: Output correct for input = 010
#   Time: 30 ns Iteration: 0 Instance: /testbench
# ** Note: Output correct for input = 011
#   Time: 40 ns Iteration: 0 Instance: /testbench
# ** Note: Output correct for input = 100
#   Time: 50 ns Iteration: 0 Instance: /testbench
# ** Note: Output correct for input = 101
#   Time: 60 ns Iteration: 0 Instance: /testbench
# ** Note: Output correct for input = 110
#   Time: 70 ns Iteration: 0 Instance: /testbench
# ** Note: Output correct for input = 111
#   Time: 80 ns Iteration: 0 Instance: /testbench
V$IM 3>
```

**Figure 4: Simulation Results with Assert Statements**