## **Datapath Verification Report**

## Component


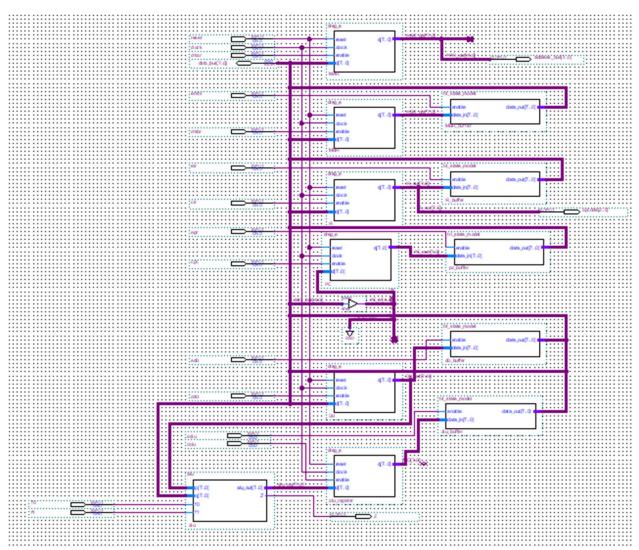


Figure 1: Datapath Schematic

The purpose of this learning activity is to create the datapath component for the cpu. The datapath takes in 16 inputs and outputs 3 values. Among the 16 inputs, one input is the *reset* and another is the *clock*. Then the rest of the inputs of are instructions. Figure 1 highlights the datapath schematic which is composed of 6 registers with 5 tri-state components and the alu.

## **Verification Tests**

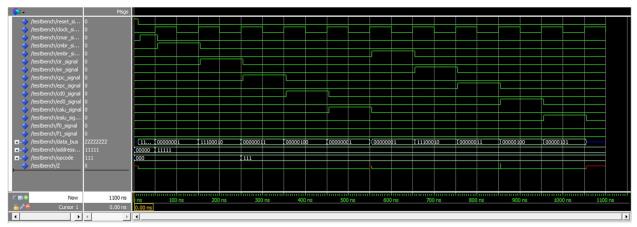

**Figure 2: Verification Tests** 

Data Bus	Register	Read Value
11111111	MAR	11111111
00000001	MBR	0000001
11100010	IR	11100010
00000011	PC	00000011
0000001	fPQ (ALU register)	00000101
00000100	D0	00000100

**Figure 3: Truth Table from Verification Tests** 

```
# ** Note: Output correct for reading from MBR register, data bus output should be 00000001
# Time: 650 ns Iteration: 1 Instance: /testbench
# ** Note: Output correct for reading from IR register, data bus output should be 11100010
# Time: 750 ns Iteration: 1 Instance: /testbench
# ** Note: Output correct for reading from PC register, data bus output should be 00000011
# Time: 850 ns Iteration: 1 Instance: /testbench
# ** Note: Output correct for reading from D0 register, data bus output should be 00000100
# Time: 950 ns Iteration: 1 Instance: /testbench
# ** Note: Output correct for reading from fPQ register, data bus output should be 00000101
# Time: 1050 ns Iteration: 1 Instance: /testbench
```

**Figure 4: Verification Tests with Assertion Statements** 

Figure 2 - 4 illustrate the verification process for the datapath. I tested if I could write to and read from each register using the *data bus* input and output. Figure 3 illustrates the data that were

loaded into each register. For fPQ, the values are loaded into the alu and alu register where P comes from the D0 register and Q comes from the databus. In this case, P is 00000100 and Q is 00000001, so the output from the alu register should be 00000101. Since all the test cases are passed, the datapath schematic is correct.